

Basic programming using VHDL

Index


1. Introduction
2. Basic structure of digital circuit design with VHDL
3. Basic features of VHDL

1:

Introduction


Standard wired logic

Digital logic function


 


"Black box" with I / O True table

Sum of products Simplification

 

CMOS NAND gate

  

X ₁	X ₂	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	1
1	0	Off	On	On	Off	1
1	1	Off	Off	On	On	0

Based on transistors

Logic chips standard

Fixed logic!

Need for user-defined layouts

Programmable logic (I)

- Programmable logic allows the user to define the function carried out by a circuit.
- Programmable logic is based on programmable devices, where you can define their function, unlike standard wired circuits, which have a fixed function.


To define the functionality of these programmable devices, we use Hardware Description Languages, HDL

Programmable logic (II)

- The HDL program is designed for the desired functionality.
- We simulate the program to verify proper operation (waveforms ...).
- We synthesize the program. A synthesis software translates the program into logic elements (gates ...), and then, it implements the circuit according to the programmable technology under use.
- The result (file .bit ...) is uploaded in the programmable device.
- Different types of programmable devices:
 - PLD, Programmable Logic Device
 - ASIC, Application Specific Integrated Circuit (CUSTOM)
 - FPGA, Field Programmable Gate Array

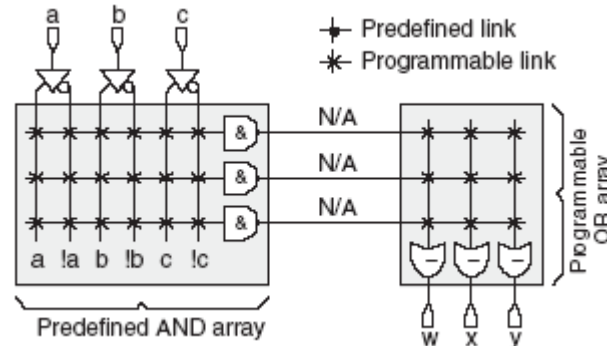Example of programmable logic device: PLD

- Groups of ANDs and ORs linked by potential links:
- programmable links
- reconfigurable links
- different types of PLDs, eg: SUM OF PRODUCTS:




logical function


$$y = (a \& b \& c)$$

$$x = (a \& b \& c) | (\bar{b} \& \bar{c})$$




$$w = (a \& c) | (\bar{b} \& \bar{c})$$

 


Sum of products

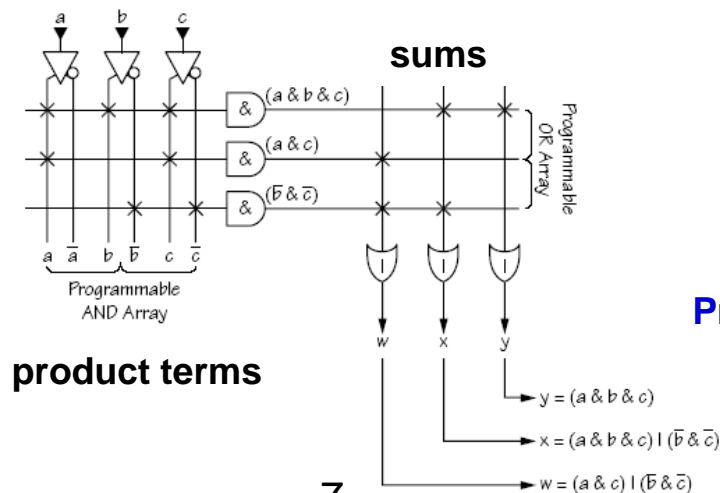

Programmable logic devices

   

 Limited complexity: thousands of doors
Cheap
Easy of design
<u>RE</u> programmable



Higher complexity: millions of doors
Very expensive for small amounts (it is necessary to manufacture a <i>mask</i> for the programming). Manufactured in a Custom way (Custom, eg. for very high speed, low consumption...)
Long & complex
<u>DO NOT RE</u> programmable, high risk of failures of design

Introduction to VHDL language

- VHSIC: (Very High Speed Integrated Circuit)
Hardware Description Language
- An standard industrial language of IEEE for the description of hardware.
- A high level language for the simulation, and synthesis and implementation of programmable circuits.

History of VHDL

- 1980: The Department of Defense of US created a project to develop a new standard for the description of hardware within the VHSIC (Very High Speed Integrated Circuit) program.
- 1982: Accepted by Intermetrics, IBM and Texas.
- 1985: Version 7.2, public.
- 1987: The IEEE Institute confirms the standard as 1076 (VHDL-87).
- 1993: The VHDL language was revised and expanded as standard 1076'93 (VHDL-93)

2:

Basic structure of digital circuit design with VHDL

VHDL: design units

Entity

- Defines the external interface of the model

LOGICAL SYMBOL

Architecture

- Defines the internal functionality of the model

CIRCUIT LAYOUT

Configuration

- It is used to match an architecture with an entity

ENTITY <- -> Architecture


Library

- Saved set of components

PACKAGES (STATEMENT and BODY)

Entity and architecture: 1st level of abstraction

Abstraction: black box

 

Interface: inputs and outputs (ports)



Entity and architecture

- A hardware unit is displayed as a "black box"
 - The interface of the black box is completely defined.
 - The inside part is hidden.
- In VHDL the black box is called entity.
 - The **ENTITY describes the I / O** of the design
- To describe its operation an implementation called architecture is associated
 - The **ARCHITECTURE describes the content** of the design.

PORTS of an entity

Interface of the device



Ports: inputs and outputs



Ports = communication channels


Each of the possible connections is called a PORT and comprises:

- A **name**, which must be unique within the entity.
- Some characteristics such as:
 - the direction of the data flow, input, output, which is known as **MODE** of the port.
 - the values that the port can take, '0', '1', 'Z', etc, these possible values depend on what is called **TYPE** of signal.


PORTS: Modes of a port

Mode of ports

 It indicates the direction and whether the port can be read or written within the entity.




 - **IN** A signal entering the entity. The signal can be read but not written.



- **OUT** A signal that goes out of the entity. The signal can not be read within the entity.
- **OTHERS...**

Structure of a VHDL design

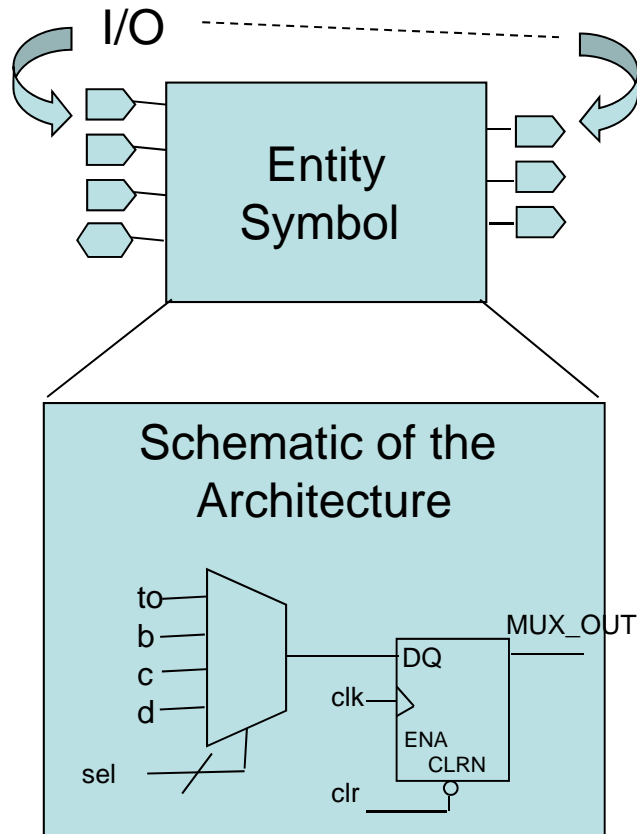


```
ENTITY IS entity_name
    port declaration
END entity_name;
```

```
my_arq_name OF ARCHITECTURE IS my_entity_name
```

```
Declaration of:
constants
internal signals
components
```

```
BEGIN
    signal assignments
    processes
    component instances
END my_arq_name;
```


Architecture

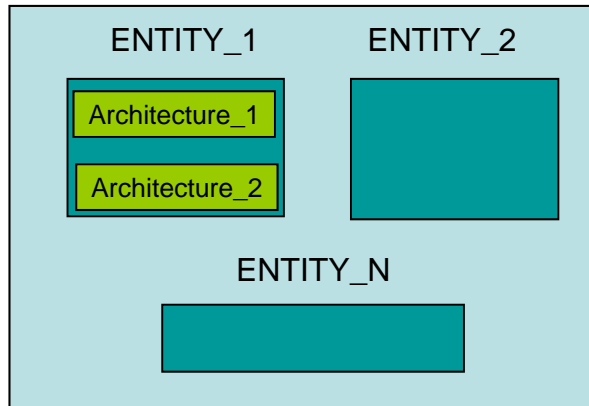

- The architecture describes what is inside the entity, ie, the contents of the black box.
- An entity can be described with different models of architecture: structural / RTL / behavioral.

```
ARCHITECTURE my_arq_1 of my_entity_name is  
  
    declarations  
  
begin  
  
    architecture instructions  
  
end my_arq_1;
```

Libraries

```
LIBRARY <name>
```

name is a symbolic name
defined by the compiler.

```
USE lib_name.pack_name.object;
```

ALL is a reserved word.

```
Library IEEE;
```

```
USE
```

```
ieee.std_logic_1164.all;
```

A library contains a package or a collection of packages (a way of storing information).

Libraries with resources:

- Standard Package

- Packages developed by IEEE

- Packages developed by
integrated circuit manufacturers

- Packages developed by the user

Working Library: WORK

Library where the current design
unit is compiled.

3:

Basic features of VHDL

Type of data

- A TYPE is the definition of the possible values that an object can take
- VHDL is a strongly typed language:
 - Objects are always assigned a type when declared
 - Assignments can only be made between objects of the same type

Predefined basic types

Types IEEE-1076

- **BIT**: only the values '0' or '1' are allowed. For digital signals.
- **BIT_VECTOR**: A one-dimension array (vector) of bits. To model buses.
- **INTEGER**: Integer type. Used as an index value in loops, constants or generic values.
- **BOOLEAN**: Logical type. It can take the values 'TRUE' or 'FALSE'
- **REAL**: For floating point numbers.
- **ENUMERATED**: Enumeration. User-defined values set. For example:
TYPE my_state IS (start, slow, fast).
- **STD_LOGIC / STD_LOGIC_VECTOR**

Type STD_LOGIC

- The two BIT values are not enough to model all the states of a real digital signal.
- The package `IEEE.standar_logic_1164` defines the type `std_logic`, which represents all the possible states of a real signal:

0	Output of a gate with low logic level
1	Output of a gate with high logic level
L	0 weak, pull-down resistor
H	1 weak, pull-up resistor
X	Unknown strong, short-circuited output
W	Unknown weak, short-circuited output
U	Uninitialized
Z	High impedance
-	No matter, used as a wildcard for synthesis and implementation

Type STD_LOGIC_VECTOR

- To describe buses we use `std_logic_vector`, which it is an array of `std_logic`.
- The types `std_logic` and `std_logic_vector` are industry standards.
- All the values are valid in a VHDL simulator, however only '0', '1', 'Z', 'L', 'H' and '-' are recognized for synthesis and implementation.
- Notation:
 - 1 bit: single quote (')
 - Multiple bits: double quotes (")

Operators defined in VHDL

- **Logic**
and
or, nor
XOR, XNOR
- **Relational**
= equal
/= Different
< Lower than
<= Lower than or equal
> Greater than
> Greater than or equal
- **Miscellaneous**
abs absolute value
** exponentiation
not negation (unit)
- **Addition**
+ add
- subtraction
& Concatenation of vectors
- **Multiplicative**
* multiplication
/ division
rem rest
mod modulus
- **Sign** (Unit)
+, -
- **Shift** (Bit_vector)
sll, srl, sla, sra, rol, ror

More on operators

- Not all operators are defined for all data types
- In particular, for `std_logic` / `std_logic_vector` we must get them from the standard libraries:
 - `std_logic_signed`
 - `std_logic_unsigned`
 - `std_logic_arith`
- Example of using the concatenation operator:

```
signal a: std_logic_vector (3 downto 0);
signal b: std_logic_vector (3 downto 0);
signal c: std_logic_vector (7 downto 0);
a <= "1100";
b <= "1001";
c <= a&b; - c = "11001001"
```

Objects available in VHDL

Constant: It is an association of a name to a fixed value.

```
constant pi: real: = 3.1416;
```

Variable: Is a temporal and local storage of data visible only within a process. Its value is immediately changed by an assignment (`:=`).


Signal: Is the modeling of a cable, which can connect ports (I / O) of entities and also connect processes within the architecture. It is a waveform that changes over time, so the assignment (`<=`) is not immediate, it is effective only when time goes on.

```
signal led: std_logic;
```

```
led <= '1';
```

Concept of signal

 
```
signal alarm: bit: = '0'; --Initial value in testbench  
...  
alarm <= '1' after 20 ns, '0' after 40 ns,  
        '1' after 60 ns;
```



Declaration of signals

Interconnection of components or processes
 
```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY my_design IS  
PORT(a, b, c, d: IN STD_LOGIC;  
      result: OUT STD_LOGIC);  
END my_design;  
  
ARCHITECTURE logic OF my_design IS  
  
  signal tmp: STD_LOGIC;  
  
BEGIN  
  
  tmp    <= a or b;  
  result <= (tmp and not (c xor d));  
  
END logic;
```




a, b, c, d and result are default signals (ports), while tmp needs to be declared as it is an internal signal.

Basic elements of VHDL

Processes: Consist of instructions executed and evaluated within it sequentially. Several processes are evaluated concurrently, but once a process starts the execution of its sequential instructions time does not go on, No signals are assigned until the process ends

Concurrent instructions: the ones in the architecture outside any process, and they are evaluated concurrently.

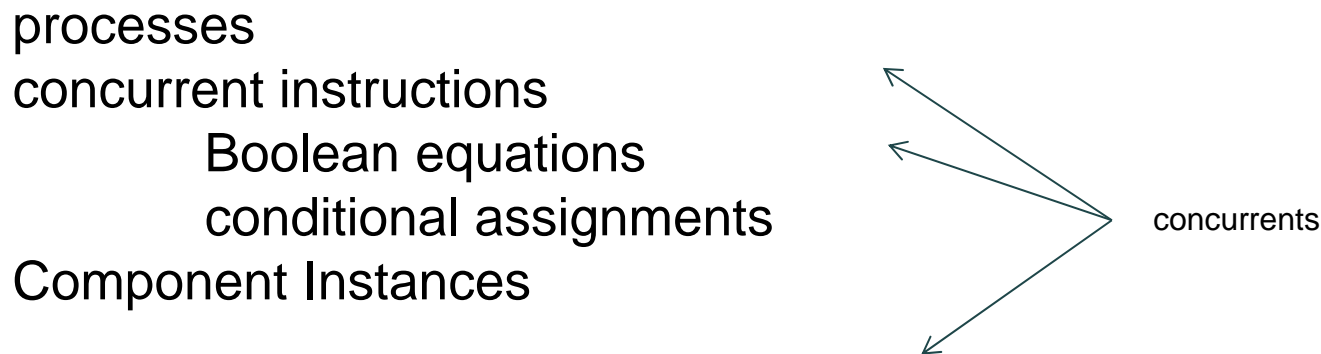Component Instances: Evaluated concurrently.



Concurrency in VHDL

```
architecture my_arch of my_ent is
begin
  c <= a and b;
  d <= c when led = '1' else 'Z';
} concurrent assignments

  seq: process (clk, reset)
  begin
    .
    .
    .
  } sequential instructions
end process;
```

- VHDL supports the notion of "concurrent execution".

- The elements used to describe concurrency within an architecture are:

- instances
- concurrent instructions
- processes

```
optional label → Proc_A: process (sig_1, sig_2)
                    } List of sensitivity
                    begin
                    } process body: sequential instructions
                    }
end process;
```

declarative region of process


- The relative order of processes and concurrent assignments within an architecture is not relevant.

- Signals are used to control the activation of processes through the sensitivity list.

```
end my_arch;
```

Concurrent instructions

```
d <= a AND b;  
e <= d NOR c;
```

 


concurrent assignments

- An instruction is executed only when any of its inputs changes.
- The assignment of the new values is performed once all the instructions whose inputs have changed are executed.
- If as a result of the new value, any of the inputs of another instruction changes, the instruction is executed.

Processes

Processes

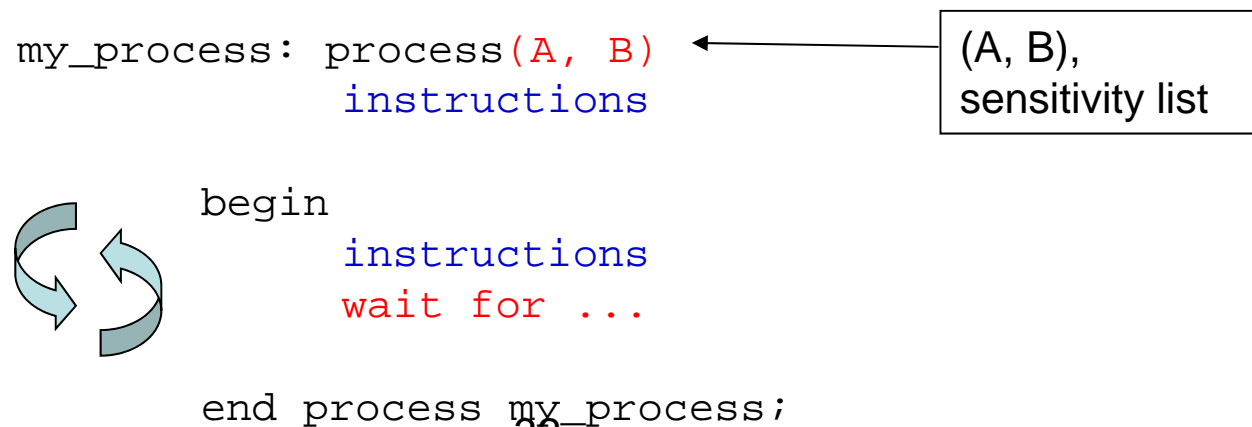- A VHDL model can be considered as a set of processes executed in parallel.
- Every process must have a sensitivity list, which is a set of signals that activate the process when a change occurs in any of them.



Sequential instructions: Processes

- Instructions within a process are evaluated sequentially.
- A process can be either *active* (AWAKE) or *inactive* (Asleep)
 - When a signal in the sensitivity list changes its value, the process proceeds to active
 - When all the instructions have been evaluated, the process becomes inactive
- Time goes on only when the process becomes inactive.

```
- Process
PROCESS (Sensitivity list)
    Constants declarations
    Variables declarations
    BEGIN
        Sequential instruction 1
        sequential instruction 2
        ...
        sequential instruction n
    END PROCESS;
```


Signal assignment in processes

- Important!

Assignments to signals within processes are only executed when the process finishes.

- Why?:
 - Signals model physical connections, and therefore they have to take into account the value, but also the time
 - Time has to go on for a cable to change its value
 - Likewise, for a signal to change its value, time has to go on
 - Time only goes on when the process finishes

Sequential instructions: eg. MUX process

 

```
mux: PROCESS (a, b, sel)
BEGIN
    IF sel = '0' THEN
        x <= a;
    ELSE
        x <= b;
    END IF;
END PROCESS mux;
```

Sequential instructions: IF-THEN-ELSE

```

PROCESS(Sela, Selb, a, b, c)
BEGIN
  IF Sela = '1' THEN
    result <= a;
  ELSIF Selb = '1' THEN
    result <= b;
  ELSE
    result <= c;
  END IF;
END PROCESS;


```

IF-THEN-ELSE:

```

IF <Condition1> THEN
  {instructions}
ELSIF <Condition2> THEN
  {instructions}
  .
  .
  .
ELSE
  {instructions}
END IF;

```

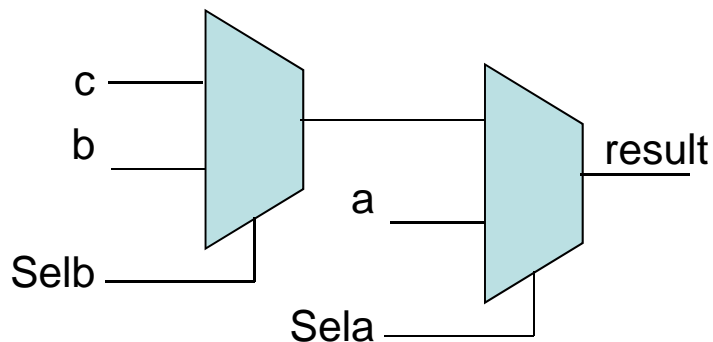

Priority: Conditions are evaluated in order from top to bottom.

The first condition TRUE causes the associated instructions to be evaluated. If all conditions are false associated instructions to ELSE are evaluated

Sequential instructions: CASE

```

PROCESS(sel, a, b, c, d)
BEGIN
    CASE sel IS
        WHEN "00" =>
            result <= a;
        WHEN "01" =>
            result <= b;
        WHEN "10" =>
            result <= c;
        WHEN OTHERS =>
            result <= d;
    END CASE;
END PROCESS;


```

CASE:

```

CASE <Expression> IS
    WHEN <Condition1> =>
        {instructions}
    WHEN <Condition2> =>
        {instructions}
        .
        .
        .
    WHEN OTHERS =>
        {instructions}
END CASE;

```

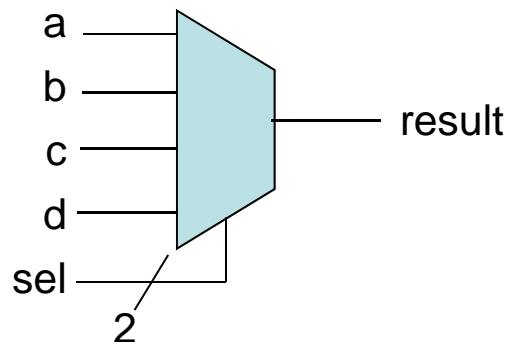


Conditions are evaluated once, no priority.


The OTHERS clause is used to assess unspecified cases.

Hierarchical design

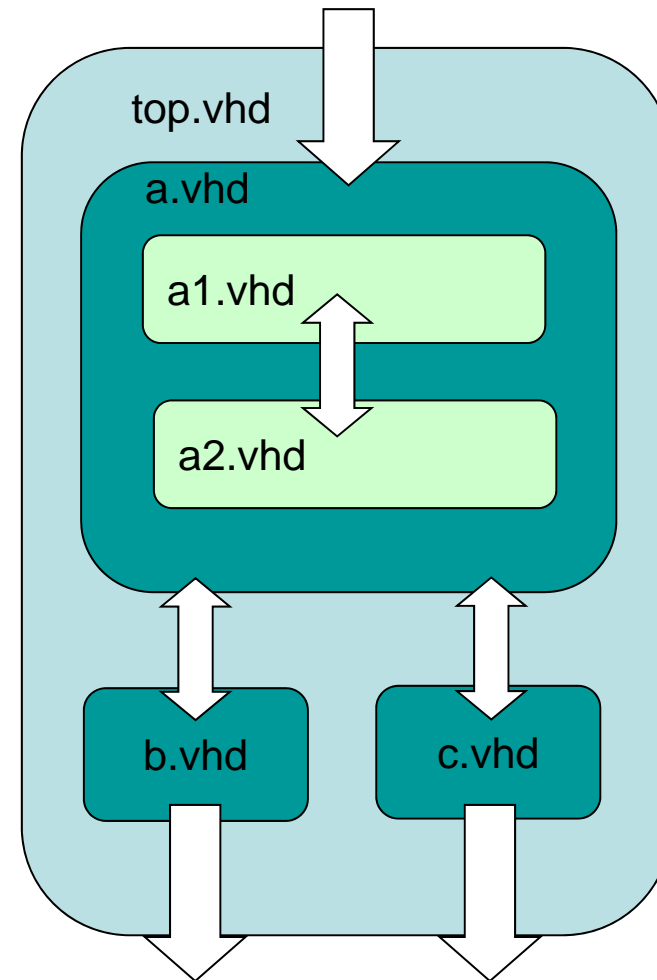- Small components are used as elements of larger components,
- It is essential for code reusability
- It generates more readable and more portable designs



TREE of the hierarchy

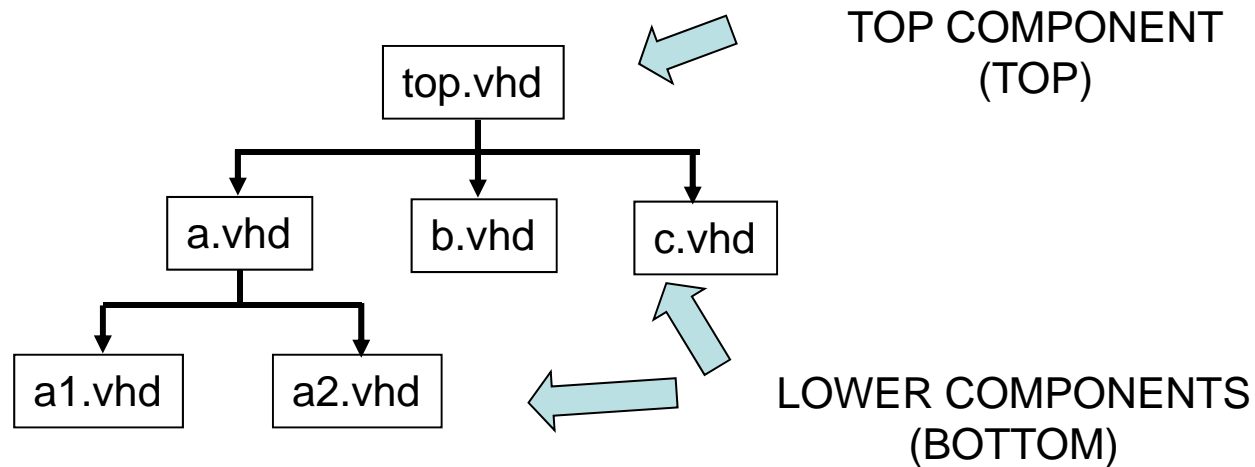

Each component of the hierarchy is a VHDL file, and has its own:

- Entity (logical symbol)
- Architecture (design of the circuit)

Declaration of components

- Before you can use a component, you must declare it
 - Specify ports (PORT)
- Once the component is instantiated, the ports of the instance are connected to the circuit signals using PORT MAP

How to instantiate a component

```
ENTITY top_ent IS
```

```
    PORT ();
```

```
END top_ent;
```

```
ARCHITECTURE my_hier OF top_ent IS  
    signal a, b, c, d: std_logic;
```


```
        COMPONENT my_comp PORT  
            (my_input: IN std_logic;  
             my_output: OUT std_logic);  
        END COMPONENT;
```

```
begin
```

```
    U1: my_comp PORT MAP  
        (my_input => a,  
         my_output => b);
```

```
    U2: my_comp PORT MAP  
        (my_input => c,  
         my_output => d);
```

```
end my_hier;
```

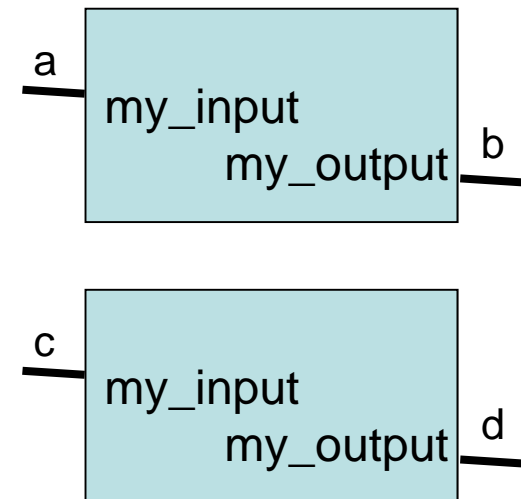

Configuration

A configuration is a unit of design

They are used to:

- Associate an entity with an architecture

Extensively used in simulation environments

- It provides a quick and flexible way to **try out different alternatives for the design (different architectures)**

Limited or not supported in synthesis environments and implementation

```
CONFIGURATION my_config OF my_ent IS
  FOR my_arqui

  END FOR;
END my_config;
```